

Advanced Amateur Radio Licence

Rupert Brooks

April 25, 2013

Outline

Prolegomena

- Basics

RLC Circuits

- Time Constant

- Reactance

Power Supplies

- Rectifiers

- Filters

- Terms and concepts

- ▶ Farad: Capacitance, $1F = 1C/V = 1s^4 \cdot A^2/m^2 \cdot kg$
- ▶ Henry: Inductance, $1H = 1Wb/A = 1V \cdot s/A = 1\Omega \cdot s$
- ▶ Hertz: Frequency, f , also angular frequency ω in rad/s
- ▶ $1Hz = 2\pi rad/s$; $f = 2\pi\omega$

- ▶ Skin Effect: RF current in a conductor flows along the outside

Time Constant

- ▶ Time constant:
 - ▶ RC time required for voltage to reach 63.2% of equilibrium
 - ▶ RL time required for current to reach 63.2% of equilibrium
- ▶ Why 63.2%? Because it is an exponential function.

$$v(t) = v_e e^{-t/RC}$$

$$I(t) = I_e e^{-tL/R}$$

Note: These are both for decay. For rise, use $1 - e^{-t/RC}$

Time Constant

Time constants	e^{-t}	$1 - e^{-t}$
0	1.000	0.000
1	0.368	0.632
2	0.135	0.865
3	0.050	0.950
4	0.018	0.982
5	0.007	0.993

- ▶ Circuitlab RC <https://www.circuitlab.com/circuit/ga5y34/simple-rc/>
- ▶ Circuitlab RL <https://www.circuitlab.com/circuit/veg4ma/simple-rl/>

Reactance

- ▶ In a pure resistance, current is in phase with voltage.
- ▶ In a pure capacitance, current leads voltage by 90°
- ▶ In a pure inductance, voltage leads current by 90°
- ▶ Reactance and resistance can be viewed as a complex number.
Impedance is the magnitude of this number.

Capacitive Reactance

$$X_c = \frac{-j}{2\pi fC}$$

Inductive Reactance

$$X_i = j2\pi fL$$




Impedance, $Z = \sqrt{R^2 + X^2}$

Image taken from

<http://electronicsclub.info/impedance.htm>


Resonance

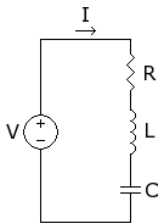- ▶ Capacitive and Inductive reactances oppose.
- ▶ The frequency at which they exactly cancel is the resonant frequency.
- ▶ $f = \frac{1}{2\pi\sqrt{LC}}$
- ▶ The resonant frequency can be altered by resistance in some configurations, but not in pure series or pure parallel.



Attrib:

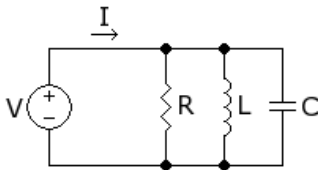http://en.wikipedia.org/wiki/File:RLC_series_circuit.png



Attrib:

http://en.wikipedia.org/wiki/File:RLC_parallel_circuit.png

Q factor

- ▶ Indication of 'quality' of a resonator.
- ▶ High Q indicates small bandwidth, and low damping.
- ▶ $Q = \frac{1}{F_b}$
- ▶ Series $Q = \frac{X}{R}$, Parallel $Q = \frac{R}{X}$
- ▶ F_b is width between the -3dB points

Examples on circuitlab

- ▶ `https://www.circuitlab.com/circuit/5xp69v/series-rlc/`
- ▶ `https://www.circuitlab.com/circuit/tgbk77/parallel-rlc/`

Rectifiers

- ▶ Half Wave
- ▶ Full Wave
- ▶ Bridge

Note that the full wave is two diodes, one from each side of a center tapped transformer. Thus the full wave has half the output voltage of a bridge (4 diodes).

Also, don't be tricked by the ripple frequency - it's double the supply frequency for full and bridge rectifiers.

Diodes should be rated with a PIV of 2.8 times the transformer secondary. Just memorize it.

They state you may put bypass resistors and capacitors around the rectifiers to guard against voltage spikes. I have not seen this.

Supply filters are classified by the first component after the rectifier.

- ▶ Choke input
- ▶ Capacitor input

Capacitor input has higher output voltage, but choke input can handle higher loads.

The questions state that choke input can give better regulation.

Terms and concepts

- ▶ *Bleeder Resistors* - maintain a minimum current draw, often necessary on choke input filtered systems
- ▶ *Linear vs Switching* supplies
- ▶ *Zener diodes* - often used as voltage reference
- ▶ *Remote sensing*. It may be necessary to take feedback from near the load, if the voltage may be drawn down over long supply leads.
- ▶ *dynamic regulation* Managing short term changes in load resistance.
- ▶ *static regulation* Managing long term changes in load resistance.

Linear regulators

- ▶ May be configured as series (series with load) or shunt (parallel with load) configuration.
- ▶ Often packaged as a *three terminal regulator*.
- ▶ Internally, this contains
 - ▶ voltage reference
 - ▶ error amplifier
 - ▶ sensing resistors and transistors
 - ▶ pass element
- ▶ and is characterized by
 - ▶ min / max input voltage
 - ▶ max output current and max output voltage.