

Advanced Amateur Radio Licence

Rupert Brooks

May 1, 2013

Outline

Components and circuits

- Active Components
- Transistor Circuit configurations
- Amplifier Characteristics
- Filters
- Continued

Meters and Measurement

- ▶ Diode: Electrons will flow in a vacuum from a hot cathode to an anode, but not the other way.
- ▶ Triode: Adding a grid in between at a variable voltage, allows to control a large current with a small current.
- ▶ Tetrodes and pentodes: Operation of the triode has some linearity and other problems. Tetrodes and pentodes add other grids (screens) to clean this up (roughly speaking).
- ▶ The Cathode may be heated separately by the filament, or heater.
- ▶ All this metal junk may have stray capacitance, and require *neutralization* in RF work.

Grounded Grid amplifier

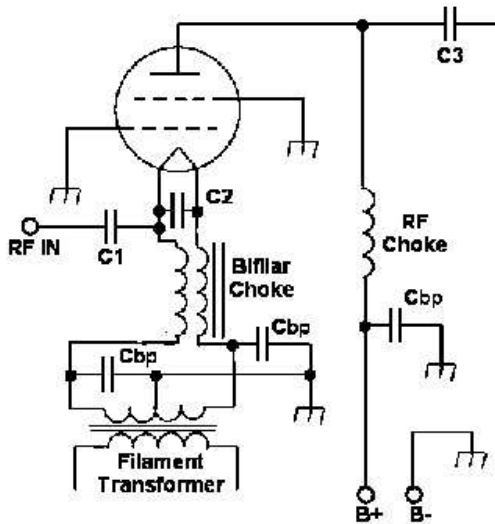



Image taken from

<http://wb0nni.dakotamade.com/ggbasic.html>. See there for discussion, also the answer to the grounded grid questions

Semiconductors

- ▶ Semiconductors are materials such as silicon, germanium or gallium arsenide (GHz freq).
- ▶ Note that pure Si is an insulator.
- ▶ When doped, there are either extra electrons (N-type), or missing electrons (holes) (P-Type)

 - ▶ Hot-Carrier or Schottky - Low forward voltage drop and fast switching. Cats-whisker detector is a form of Schottky diode. Good for VHF/UHF mixers and detectors. Metal contact on a single type of doped semiconductor.



- ▶ PIN diode - Have a layer of intrinsic semiconductor between the P and N layers. Low capacitance and fast switching. Good for RF switch
- ▶ Point-contact diode: Group III metal makes a sharp contact on N-type semiconductor. Some metal dissolves into the semiconductor generating a small P region. The 1N34 Germanium diode is an example, makes good RF detectors.

- ▶ Varactor diode - varies internal capacitance with applied voltage



- ▶ Zener diode - regulates voltage through breakdown at a specific voltage level via the Zener mechanism, and some avalanche mechanism.
- ▶ Avalanche diode - (not on exam). Can suppress voltage spikes through avalanche breakdown - not as regulated as Zener.


Bipolar Junction Transistor

- ▶ PNP or NPN types. Current positive to negative against the arrow.
- ▶ Allows small base-emitter current to control large collector emitter current.
- ▶ $I_e = I_b + I_c$
- ▶ Common base current gain $\alpha = I_c/I_e$
- ▶ Common emitter current gain $\beta = I_c/I_b = H_{fe}$
- ▶ Common collector current gain $\gamma = I_e/I_b$
- ▶ $\alpha = \frac{\beta}{1+\beta} = \frac{\gamma-1}{\gamma}$
- ▶ $\beta = \frac{\alpha}{1-\alpha} = \gamma - 1$
- ▶ $\gamma = 1 + \beta = \frac{1}{1-\alpha}$

Other active components

- ▶ FETs (Field Effect Transistors): A three terminal device, with source, drain and gate.
 - ▶ Enhancement mode FET: No channel, no current flows at zero voltage. Voltage must be applied to create the channel and allow current to flow.
 - ▶ Depletion mode FET: Channel, current flows with zero voltage applied. Voltage must be applied to shut it off (or encourage it)
 - ▶ Junction FET: has a PN junction to separate the gate
 - ▶ MOSFET: Metal-oxide-semiconductor separates the gate. Static sensitive.
- ▶ SCR: A three terminal (anode, cathode and gate), four layer (PNPN) device. Once triggered by gate current, behaves like a junction diode. In amateur radio, frequently used in crowbar overvoltage protection.


Common Emitter

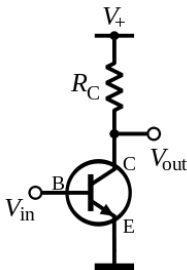

http://en.wikipedia.org/wiki/File:NPN_common_emitter.svg

- ▶ Current amplification $\gg 1$. Voltage amplification $\gg 1$
- ▶ phase reversal (180 degrees)
- ▶ similar to FET common source
- ▶ in the FET common source, the input impedance is essentially determined by the gate biasing network
- ▶ in the FET common source, output impedance is essentially determined by the drain resistor.


Common Base

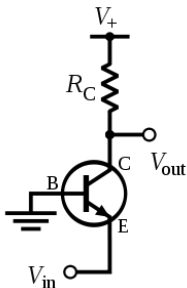

http://en.wikipedia.org/wiki/File:NPN_common_base.svg

- ▶ Current amplification < 1 Voltage amplification $>> 1$
- ▶ no phase shift
- ▶ low input impedance
- ▶ similar to FET common gate


Common collector

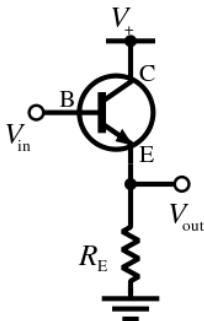

http://en.wikipedia.org/wiki/File:NPN_emitter_follower.svg

- ▶ Current amplification $\gg 1$. Voltage amplification < 1
- ▶ no phase shift
- ▶ aka emitter follower
- ▶ similar to FET common drain (source follower)


Darlington pair

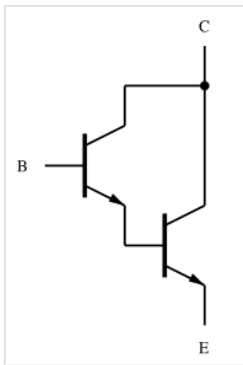

http://en.wikipedia.org/wiki/File:Darlington_pair_diagram.svg


- ▶ Current amplification $\gg 1$. Voltage amplification $\gg 1$
- ▶ high gain
- ▶ high input impedance
- ▶ low output impedance

Amplifier classes

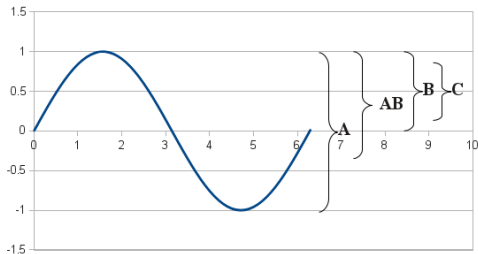

- ▶ A: full 360 of phase, most linear, least efficient
- ▶ AB: More than 180 of phase, but less than 360 (SSB)
- ▶ B: 180 of phase
- ▶ C: Less than 180 of phase. Most distortion, most efficient (CW, RTTY or FM)

Filters

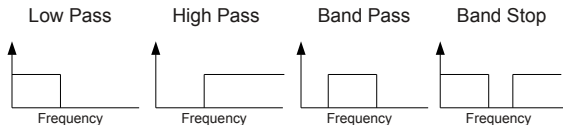


- ▶ Butterworth is flat (smooth as butter), but sacrifices steepness of skirts
- ▶ Chebyshev type I is described in the hamstudy notes (passband ripple).
- ▶ Chebyshev type II exists, has stopband ripple instead
- ▶ Both Chebyshevs accept some ripple in return for steep skirts
- ▶ Elliptic filters are a family of filters that range between Butterworth, and the two Chebyshevs at the extremes.
- ▶ Cavity filters and helical resonators are physical objects. Cavity filters have very narrow BW.

See the hamstudy notes

- ▶ Operational Amplifiers
- ▶ Mixer and frequency multiplier (explain image frequency)
- ▶ Digital Logic
- ▶ Quartz Crystals

Voltages and PEP

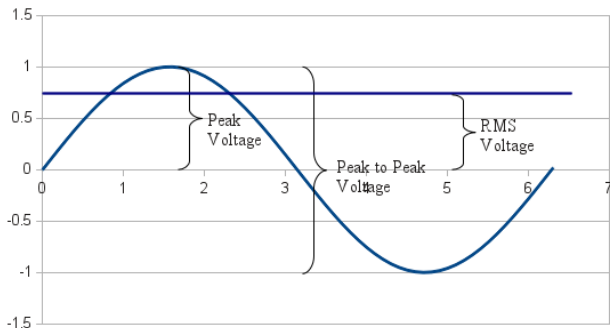

- ▶ Peak Envelope Power: $PEP = E_{RMS}^2 / R$

- ▶ For the rest of the meters, see the hamstudy notes